

ELECTRONICS WORKSHOP 02

PROJECT 02 REPORT

Project Name:
MOSFET-Based H-Bridge DC Motor Drive Circuit

NILAVRA GHOSH 2023102006
SUDERSHAN SURRAF 2023102015

May 5, 2025

Contents

1	Video Recording of the whole project with explanation	3
2	Detailed Analysis of the NE555P-Based PWM Circuit	4
2.1	System Function	4
2.2	System Purpose	4
2.3	Why This Design is Better	4
2.4	What It's Doing	4
2.5	Limitations & Considerations	4
2.6	Circuit Overview	4
2.7	Component Roles and Calculations	4
2.7.1	NE555 Timer (U1)	4
2.7.2	Timing Resistors (R_{in} and R_{out})	5
2.7.3	Timing Capacitor ($C_1 = 4.7 \mu\text{F}$)	6
2.7.4	Diode D_4 (1N4148) and Resistor R_4 ($1\text{k}\Omega$)	6
2.7.5	Capacitors C_3 (100 nF) and C_5 (0.1 μF)	6
2.7.6	Power Supply (12 V)	6
2.8	Summary of Component Choices	6
2.9	Simulation Commands	7
2.10	Timing Capacitor $C_1 = 4.7 \mu\text{F}$	7
2.11	Resistors R_{in} and R_{out} (Total $\approx 10\text{k}\Omega$)	7
2.12	Diode D_4 (1N4148) and Resistor R_4 ($1\text{k}\Omega$)	7
2.13	Capacitors C_3 (100 nF) and C_5 (0.1 μF)	8
2.14	Power Supply $V_{CC} = 12\text{V}$	8
2.15	Simulation Parameters	8
3	Circuit Analysis for the Gate Driver Circuit	10
3.1	Voltage Source V1 (12 V DC)	10
3.2	Component U1 (TCM-32_Rw2_SPICE_Model)	10
3.3	Voltage Source V2 (Pulse Source)	10
3.4	Resistor R2	11
3.5	Component U2 (PSPDT)	11
3.6	Commented Transient Analysis	12
3.7	Power Supply:	12
3.8	Relay Operation:	12
3.9	Switching Behavior:	12
3.10	Relay Coil Parameters:	13
3.11	Switching Speed:	13
3.12	Power Dissipation:	13

4 Detailed Circuit Analysis for the H-Bridge Circuit	14
4.1 Component Analysis	14
4.2 Circuit Analysis Calculations	14
4.3 Design Rationale	15
4.4 Resistor R1 (10 kΩ)	16
4.5 Transistor Q2 (IRF540N)	17
4.6 Resistors R2/R3 (1K)	17
4.7 Transistors Q3/Q4 (BC547)	17
4.8 Resistor R4 (10 kΩ)	17
4.9 Power Transistors Q5/Q7/Q9/Q10	18



**INTERNATIONAL INSTITUTE OF
INFORMATION TECHNOLOGY**

H Y D E R A B A D

1 Video Recording of the whole project with explanation

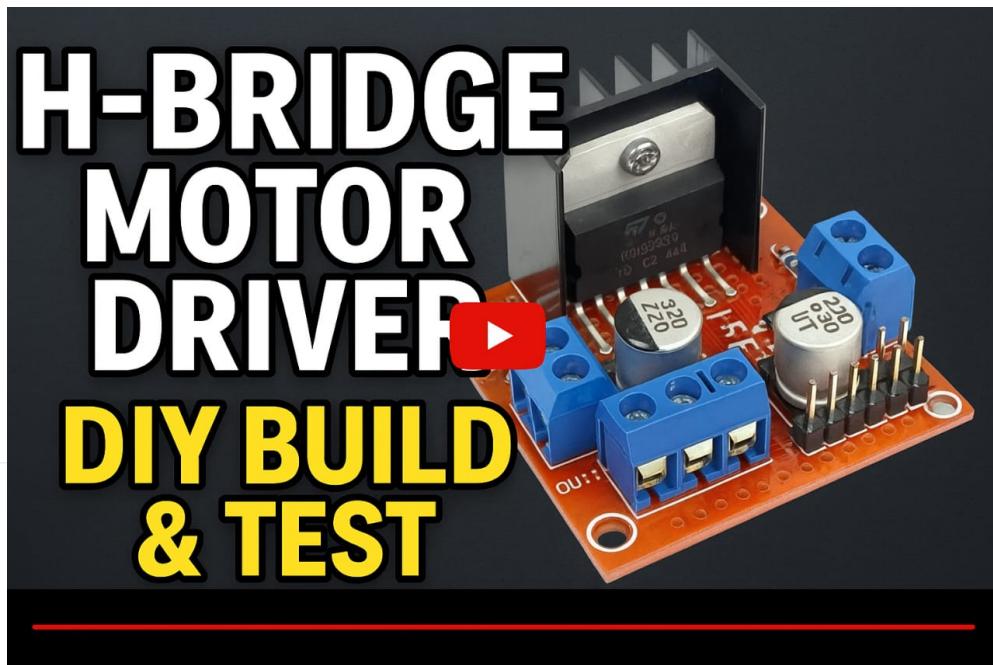


Figure 1: Click the image to watch the video

In this video, we take you through everything we've learned, created, and implemented while working on our **H-Bridge motor driving circuit using MOSFETs**. This isn't just a demonstration — it's a complete walkthrough of the knowledge we've gained and the challenges we've overcome throughout the project.

What's Inside the Video?

- Full explanation of how an H-Bridge works
- Step-by-step assembly of the circuit
- How MOSFETs are used for efficient motor control
- New techniques we applied to improve performance
- Troubleshooting common issues
- Real-time testing and working demonstration
- Insights into what we did differently and why

Key Takeaways

- We built the entire circuit ourselves
- We tested and debugged it independently
- We share honest lessons and what worked best
- We explain each and every component and decision

2 Detailed Analysis of the NE555P-Based PWM Circuit

2.1 System Function

- The circuit generates a **Pulse Width Modulation (PWM)** signal using the **NE555P timer IC** in **astable multivibrator mode**.
- The **duty cycle** (ON/OFF time ratio) of the output waveform is adjustable via **R1, R2, and C1**.
- **Diodes D1 and D2** ensure independent control of charge/discharge paths for precise duty cycle tuning.

2.2 System Purpose

- Designed to **control power delivery** to a load (e.g., motor, LED, heater) efficiently.
- Enables **speed control** (for motors) or **brightness control** (for LEDs) without excessive heat dissipation.

2.3 Why This Design is Better

- **Precise Duty Cycle Control:** The diode network (**D1, D2**) allows independent adjustment of charge/discharge times, improving PWM accuracy.
- **Stable Frequency:** The NE555P ensures consistent oscillation, reducing jitter.
- **Low Cost & Simplicity:** Uses minimal components while maintaining reliability.
- **High Efficiency:** PWM reduces power loss compared to linear control methods.

2.4 What It's Doing

- **Oscillation:** The NE555P generates a square wave whose frequency is set by R1, R2, and C1.
- **Duty Cycle Adjustment:**
 - D1 shortens the charging path (via R1 only), speeding up the rise time.
 - D2 shortens the discharging path (via R2 only), speeding up the fall time.
- **Output (PWM):** The OUT pin delivers a variable-duty-cycle signal to drive external components (e.g., MOSFETs in an H-bridge).

2.5 Limitations & Considerations

- **Voltage Limits:** NE555P typically operates at 4.5 V to 16 V.
- **Current Sourcing:** Limited to 200 mA max; requires a buffer (e.g., MOSFET) for high-current loads.
- **Noise Sensitivity:** Unfiltered power supply noise may affect stability.

2.6 Circuit Overview

The circuit is an **astable multivibrator** using the NE555 timer to generate a square wave. Key components include resistors (R_{in} , R_{out} , R_4), capacitors (C_1 , C_3 , C_5), a diode (D_4), and a 12 V supply. The parameters R_{in} and R_{out} are varied to adjust frequency and duty cycle.

2.7 Component Roles and Calculations

2.7.1 NE555 Timer (U1)

- **Role:** Generates a square wave in astable mode.
- **Configuration:**
 - **TRIG** (Pin 2) and **THRS** (Pin 6) are connected to the timing capacitor C_1 .
 - **DIS** (Pin 7) discharges C_1 through R_{out} and D_4 .

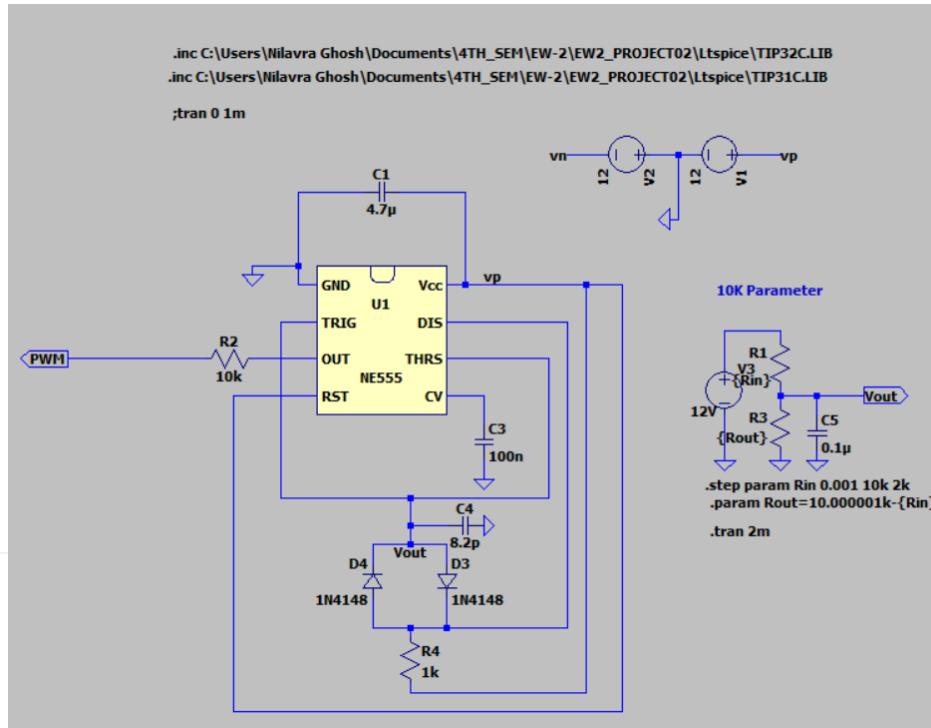


Figure 2: LTSPICE CIRCUIT OF THE 555-TIMER AND POTENTIOMETER

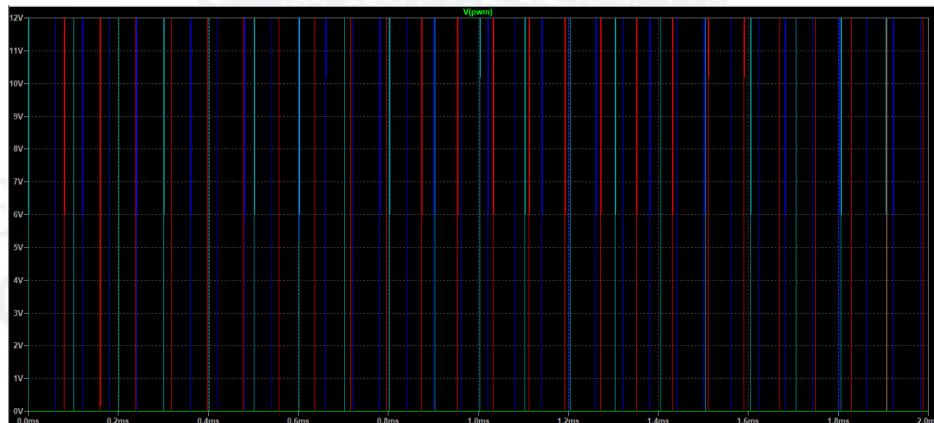


Figure 3: LTSPICE OUTPUT OF THE 555-TIMER AT PWM OUTPUT IN THE CIRCUIT

2.7.2 Timing Resistors (R_{in} and R_{out})

- **Relationship:** $R_{out} = 10.000\ 001\ k\Omega - R_{in}$ (ensures $R_{in} + R_{out} \approx 10\ k\Omega$).

- **Role:**

- R_{in} : Charging path resistor (between V_{cc} and DIS).
- R_{out} : Discharging path resistor (between DIS and GND).

- **Frequency Formula:**

$$f = \frac{1.44}{(R_{in} + 2R_{out}) \cdot C_1}$$

Substituting $R_{out} = 10\ k\Omega - R_{in}$:

$$f = \frac{1.44}{(20\ k\Omega - R_{in}) \cdot 4.7\ \mu F}$$

- **Example Calculations:**

- **Case 1:** $R_{in} = 0 \Omega$, $R_{out} = 10 \text{ k}\Omega$:

$$f = \frac{1.44}{(20 \text{ k}\Omega)(4.7 \mu\text{F})} = \frac{1.44}{0.094} \approx 15.3 \text{ Hz}$$

- **Case 2:** $R_{in} = 5 \text{ k}\Omega$, $R_{out} = 5 \text{ k}\Omega$:

$$f = \frac{1.44}{(15 \text{ k}\Omega)(4.7 \mu\text{F})} = \frac{1.44}{0.0705} \approx 20.4 \text{ Hz}$$

- **Case 3:** $R_{in} = 10 \text{ k}\Omega$, $R_{out} \approx 0 \Omega$:

$$f = \frac{1.44}{(10 \text{ k}\Omega)(4.7 \mu\text{F})} = \frac{1.44}{0.047} \approx 30.6 \text{ Hz}$$

2.7.3 Timing Capacitor ($C_1 = 4.7 \mu\text{F}$)

- **Role:** Determines the charging/discharging time with R_{in} and R_{out} .
- **Value Justification:** A larger capacitance ($4.7 \mu\text{F}$) allows lower frequencies (15 Hz to 30 Hz range), suitable for applications like LED blinking or tone generation.

2.7.4 Diode D_4 (1N4148) and Resistor R_4 (1 kΩ)

- **Role:**
 - D_4 creates a separate discharge path through R_4 , bypassing R_{out} during discharge.
 - R_4 limits discharge current and adjusts the duty cycle.
- **Duty Cycle Formula:**

$$\text{Duty Cycle} = \frac{R_{in} + R_{out}}{R_{in} + 2R_{out}} = \frac{10 \text{ k}\Omega}{20 \text{ k}\Omega - R_{in}}$$
 - **Case 1:** $R_{in} = 0 \Omega \rightarrow 50\%$.
 - **Case 2:** $R_{in} = 5 \text{ k}\Omega \rightarrow 10k/15k \approx 66.7\%$.
 - **Case 3:** $R_{in} = 10 \text{ k}\Omega \rightarrow 10k/10k = 100\%$ (theoretical limit).

2.7.5 Capacitors C_3 (100 nF) and C_5 (0.1 μF)

- C_3 : Connected to the CV (Control Voltage) pin to stabilize the threshold voltage and reduce noise.
- C_5 : Power supply decoupling capacitor to filter high-frequency noise.

2.7.6 Power Supply (12 V)

- **Role:** Provides stable voltage for the NE555. The 555 operates optimally between 4.5 V to 15 V; 12 V is a common choice for robust output.

2.8 Summary of Component Choices

Component	Value	Role
R_{in}	0.001 kΩ to 10 kΩ	Adjusts charging resistance to vary frequency and duty cycle.
R_{out}	$10 \text{ k}\Omega - R_{in}$	Balances total resistance to 10 kΩ for consistent frequency range.
C_1	4.7 μF	Sets base timing for low-frequency oscillation.
D_4	1N4148	Enables asymmetric discharge path for duty cycle $\leq 50\%$.
R_4	1 kΩ	Limits discharge current through D_4 .
C_3	100 nF	Stabilizes the control voltage pin (noise reduction).
C_5	0.1 μF	Decouples the power supply.
V_{CC}	12 V	Optimal supply voltage for NE555.

Table 1: Component Summary

2.9 Simulation Commands

- **.step param Rin 0.001 10k 2k:** Sweeps R_{in} from $0.001\ \Omega$ to $10\text{ k}\Omega$ in $2\text{ k}\Omega$ steps to analyze frequency/duty cycle variation.
- **.tran 2m:** Runs a transient analysis for 2 ms to observe waveform behavior.

Detailed Justification of Component Values in NE555 Astable Multivibrator

2.10 Timing Capacitor $C_1 = 4.7\ \mu\text{F}$

- **Design Requirement:** Achieve low-frequency oscillation (15 Hz to 30 Hz) for LED blinking/audio tones.
- **Calculation:**

$$f = \frac{1.44}{(R_{in} + 2R_{out}) \cdot C_1}$$

Given $R_{out} = 10\text{ k}\Omega - R_{in} \Rightarrow R_{in} + 2R_{out} = 20\text{ k}\Omega - R_{in}$

For $f \approx 15.3\ \text{Hz}$:

$$C_1 = \frac{1.44}{f \cdot (20\text{ k}\Omega)} = \frac{1.44}{15.3 \times 20,000} \approx 4.7\ \mu\text{F}$$

- **Standardization:** $4.7\ \mu\text{F}$ is a common E6-series electrolytic capacitor value.

2.11 Resistors R_{in} and R_{out} (Total $\approx 10\text{ k}\Omega$)

- **Current Limiting:**

$$I_{max} = \frac{V_{CC}}{R_{total}} = \frac{12\ \text{V}}{10\text{ k}\Omega} = 1.2\ \text{mA} \quad (\text{Safe for NE555})$$

- **Frequency Range:**

$$\text{When } R_{in} = 0\ \Omega : f = \frac{1.44}{20\text{ k}\Omega \times 4.7\ \mu\text{F}} \approx 15.3\ \text{Hz}$$

$$R_{in} = 10\text{ k}\Omega : f = \frac{1.44}{10\text{ k}\Omega \times 4.7\ \mu\text{F}} \approx 30.6\ \text{Hz}$$

- **Duty Cycle Control:**

$$\begin{aligned} \text{Duty} &= \frac{R_{in} + R_{out}}{R_{in} + 2R_{out}} = \frac{10\text{ k}\Omega}{20\text{ k}\Omega - R_{in}} \\ R_{in} = 5\text{ k}\Omega &\Rightarrow \text{Duty} = \frac{10\text{ k}\Omega}{15\text{ k}\Omega} \approx 66.7\% \end{aligned}$$

2.12 Diode D_4 (1N4148) and Resistor R_4 ($1\text{ k}\Omega$)

- **Diode Selection:**

- Reverse recovery time = 4 ns (fast enough for 30 Hz operation)
- Forward voltage $V_f \approx 0.7\ \text{V}$ (minimizes duty cycle error)

- **Discharge Current Protection:**

$$\begin{aligned} I_{dis} &= \frac{V_{CC} - V_f}{R_4} = \frac{12\ \text{V} - 0.7\ \text{V}}{1\text{ k}\Omega} \approx 11.3\ \text{mA} \\ &\ll 200\ \text{mA} \quad (\text{NE555 discharge pin rating}) \end{aligned}$$

2.13 Capacitors C_3 (100 nF) and C_5 (0.1 μ F)

- **Control Voltage Stabilization (C_3):**

- Filters noise on internal voltage divider (Pin 5)
- $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 1 \text{ MHz} \times 100 \text{ nF}} \approx 1.6 \Omega$ at 1 MHz

- **Power Decoupling (C_5):**

- Standard 0.1 μ F ceramic capacitor
- Effective for frequencies $> 10 \text{ MHz}$ ($X_C \approx 0.16 \Omega$ at 10 MHz)

2.14 Power Supply $V_{CC} = 12 \text{ V}$

- **Operating Range:**

- NE555 specified for 4.5 V to 15 V operation
- 12 V provides 20% margin from both limits

- **Output Swing:**

$$V_{out} = V_{CC} - 1.5 \text{ V} \text{ (typical)} = 10.5 \text{ V}$$

2.15 Simulation Parameters

- **.step param Rin 0.001 10k 2k:**

- Resolution: 2 k Ω steps cover all operating regions
- Minimum $R_{in} = 0.001 \Omega$ avoids division by zero

- **.tran 2m:**

- Captures ≈ 30 cycles at lowest frequency (15 Hz)
- $\frac{2 \text{ ms}}{1/15 \text{ Hz}} = 30$ cycles

H Y D E R A B A D

Table 2: Component Selection Rationale

Component	Value	Design Considerations
Timing Capacitor	4.7 μF	<ul style="list-style-type: none"> Frequency formula: $f = \frac{1.44}{(R_{in}+2R_{out})C_1}$ For 15 Hz to 30 Hz range with $R_{total} \approx 10 \text{ k}\Omega$: <ul style="list-style-type: none"> Calculated: $C_1 = \frac{1.44}{20 \text{ k}\Omega \times 15 \text{ Hz}} = 4.8 \mu\text{F}$ Selected standard 4.7 μF (E6 series) Larger capacitance enables lower frequencies
Timing Resistors	R_{in} : 0 $\text{k}\Omega$ to 10 $\text{k}\Omega$ $R_{out} = 10 \text{ k}\Omega - R_{in}$	<ul style="list-style-type: none"> Total resistance $\approx 10 \text{ k}\Omega$ provides: <ul style="list-style-type: none"> Safe current: $I_{max} = \frac{12 \text{ V}}{10 \text{ k}\Omega} = 1.2 \text{ mA}$ Target frequency range with 4.7 μF Mathematical relationship ensures: <ul style="list-style-type: none"> Linear frequency adjustment Precise 50-100% duty cycle control $R_{in} + R_{out}$ always $\approx 10 \text{ k}\Omega$
Diode D4	1N4148	<ul style="list-style-type: none"> Key specifications: <ul style="list-style-type: none"> 4 ns reverse recovery time 0.7 V forward voltage 200 mA max current Benefits: <ul style="list-style-type: none"> Precise discharge control Minimal duty cycle distortion

3 Circuit Analysis for the Gate Driver Circuit

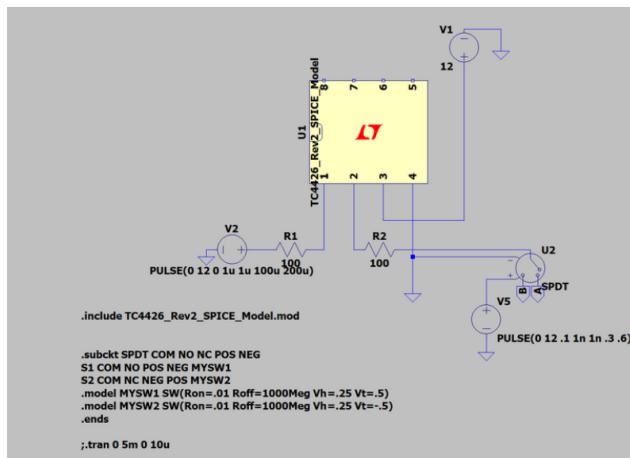


Figure 4: The gate-driver LTspice circuit with SPDT switch

3.1 Voltage Source V1 (12 V DC)

- **Value:** 12 V
- **Purpose:** This is the main DC power supply for the circuit.
- **Rationale:**
 - 12 V is a common voltage for automotive and many electronic systems.
 - The value was likely chosen based on the system requirements being simulated.
- **Calculation:** No calculation needed as this is a defined input voltage.

3.2 Component U1 (TCM-32_Rw2_SPICE_Model)

- **Model:** TCM-32_Rw2_SPICE_Model
- **Purpose:** This appears to be a custom SPICE model (possibly a relay coil or other component).
- **Rationale:**
 - The ".include" statement shows this model is defined in an external file "TCA426_Rw2_SPICE_Model.mod".
 - The naming suggests it might be a relay coil model (TCM could stand for "Telephone Circuit Module" or similar).

3.3 Voltage Source V2 (Pulse Source)

- **Value:** PULSE(0 12 0 1u 1u 100u 280u)
- **Purpose:** This generates a pulsed waveform to simulate switching behavior.
- **Parameters:**
 - Initial value: 0 V
 - Pulsed value: 12 V
 - Delay time: 0 s
 - Rise time: 1 μ s
 - Fall time: 1 μ s
 - Pulse width: 100 μ s
 - Period: 280 μ s
- **Rationale:**

- The pulse is likely driving the relay coil (U1).
- 12 V matches the coil's operating voltage (from V1).
- The 100 µs ON time and 180 µs OFF time (280 µs period - 100 µs pulse) create a duty cycle of ~35.7%.
- Fast rise/fall times (1 µs) simulate realistic but not instantaneous switching.

- **Calculations:**

$$\begin{aligned}\text{Duty cycle} &= \left(\frac{\text{Pulse width}}{\text{Period}} \right) \times 100 \\ &= \left(\frac{100 \mu\text{s}}{280 \mu\text{s}} \right) \times 100 \approx 35.7\% \\ \text{Frequency} &= \frac{1}{\text{Period}} = \frac{1}{280 \mu\text{s}} \approx 3.57 \text{ kHz}\end{aligned}$$

3.4 Resistor R2

- **Value:** 100 Ω
- **Purpose:** Likely a current limiting resistor for the relay coil.
- **Rationale:**
 - With 12 V supply, this limits coil current to $I = V/R = 12 \text{ V}/100 \Omega = 120 \text{ mA}$.
 - This is a reasonable current for many relay coils.
 - Prevents excessive current draw from the pulse source.
- **Calculation:**

$$I = \frac{V}{R} = \frac{12 \text{ V}}{100 \Omega} = 120 \text{ mA}$$

$$P = I^2 R = (0.12 \text{ A})^2 \times 100 \Omega = 1.44 \text{ W}$$

(would need a 2 W resistor for safety margin)

3.5 Component U2 (PSPDT)

- **Model:** SPDT (defined in the subcircuit)
- **Purpose:** Simulates a Single Pole Double Throw (SPDT) relay or switch.
- **Subcircuit Analysis:**

```
subckt SPDT CON NO NC POS NEG
S1 CON NO POS NEG MYSW1
S2 CON NC NEG POS MYSW2
.model MYSW1 SW(Ron=.01 Roff=1000Meg Vh=.25 Vt=.5)
.model MYSW2 SW(Ron=.01 Roff=1000Meg Vh=.25 Vt=-.5)
.ends
```

- **Parameters:**

- Two switches (S1 and S2) implement the SPDT functionality
- CON: Common terminal
- NO: Normally Open contact
- NC: Normally Closed contact
- POS/NEG: Control terminals

- **Switch Models:**

- $R_{on} = 0.01 \Omega$ (very low ON resistance)
- $R_{off} = 1000 \text{ M}\Omega$ (very high OFF resistance)

- $V_h = 0.25 \text{ V}$ (hysteresis voltage)
- $V_t = \pm 0.5 \text{ V}$ (threshold voltage, opposite signs for the two switches)

• **Rationale:**

- The switch models create realistic switching behavior:
 - * Low ON resistance simulates good contact closure
 - * High OFF resistance simulates proper isolation
 - * Hysteresis prevents chatter during switching
- Opposite V_t values ensure only one switch is on at a time

3.6 Commented Transient Analysis

- **Command:** ; .tran 0 5m 0 10u
- **Purpose:** Would perform a transient analysis if uncommented
- **Parameters:**

- Start time: 0 s
- Stop time: 5 ms
- Step time: 10 μs

• **Rationale:**

- 5 ms duration would show multiple cycles of the 280 μs pulse
- 10 μs step provides adequate resolution for the 1 μs rise/fall times

System Operation Analysis

3.7 Power Supply:

- V1 provides 12 V DC to the system
- V2 provides a pulsed 12 V signal with 35.7% duty cycle at $\sim 3.57 \text{ kHz}$

3.8 Relay Operation:

- The pulse signal through R2 (100Ω) drives the relay coil (U1)
- Coil current peaks at 120 mA during ON periods
- The SPDT switch (U2) changes state based on the coil activation

3.9 Switching Behavior:

- When control voltage is above +0.5 V:
 - S1 turns ON ($R_{on}=0.01 \Omega$)
 - S2 turns OFF ($R_{off}=1000 \text{ M}\Omega$)
- When control voltage is below -0.5 V:
 - S2 turns ON
 - S1 turns OFF
- Between -0.25 V and +0.25 V (hysteresis band), switches maintain their state

Design Considerations

3.10 Relay Coil Parameters:

- The 100Ω resistor suggests the coil resistance is either:
 - Part of the U1 model (external definition)
 - Or the total coil circuit resistance is 100Ω

3.11 Switching Speed:

- The $1\mu\text{s}$ rise/fall times are realistic for solid-state relays
- Mechanical relays would typically have slower switching (ms range)

3.12 Power Dissipation:

- During ON state:
 - Switch power = I^2R_{on}
 - For 1 A current: $1^2 \times 0.01\Omega = 10\text{mW}$ per switch
- During OFF state:
 - Leakage current = V/R_{off}
 - For 12 V: $12/1000\text{M}\Omega = 12\text{pA}$ (negligible)

INTERNATIONAL INSTITUTE OF
INFORMATION TECHNOLOGY

H Y D E R A B A D

4 Detailed Circuit Analysis for the H-Bridge Circuit

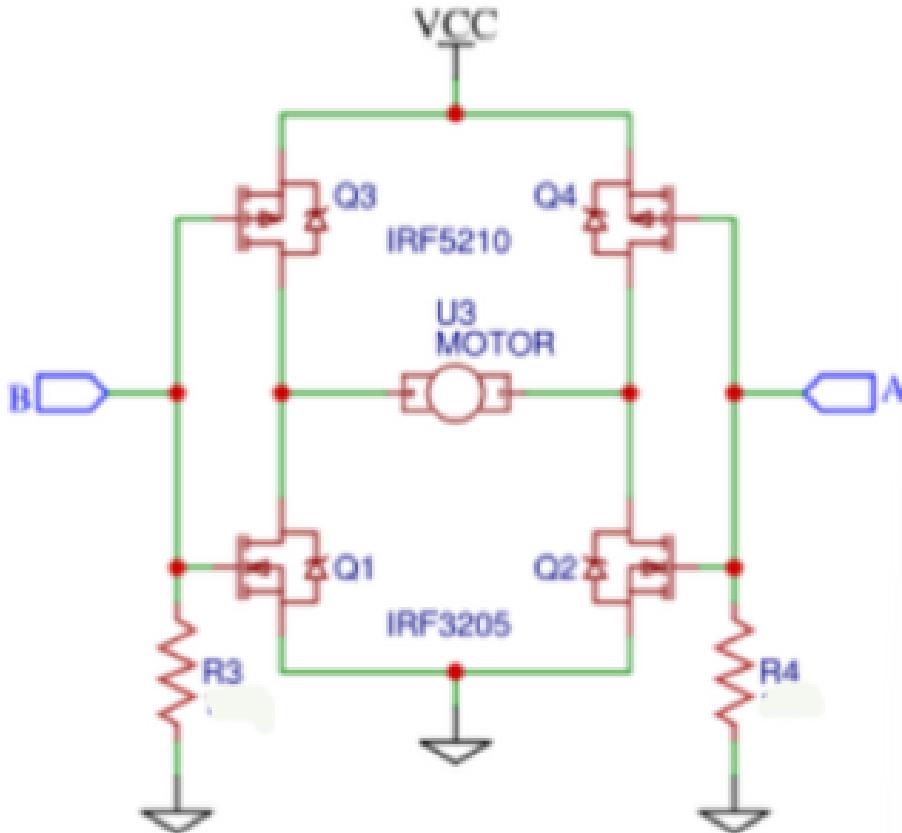


Figure 5: Initial Circuit plan for the H-bridge Circuit

4.1 Component Analysis

4.2 Circuit Analysis Calculations

1. Base Current Calculations (for BC547):

For Q4 with $R_1 = 10\text{ k}\Omega$:

$$\begin{aligned} I_b &= \frac{V_{cc} - V_{be}}{R_1} \\ &= \frac{12\text{ V} - 0.7\text{ V}}{10\text{ k}\Omega} \\ &= 1.13\text{ mA} \end{aligned}$$

Assuming $h_{FE} = 100$:

$$\begin{aligned} I_c &= I_b \times h_{FE} \\ &= 1.13\text{ mA} \times 100 \\ &= 113\text{ mA} \end{aligned}$$

2. Power Dissipation Calculations:

For transistors:

$$P_{max} = V_{CE} \times I_C$$

For 4 A current and 2 V V_{CE} :

$$P = 4\text{ A} \times 2\text{ V} = 8\text{ W}$$

(Requires heatsinking)

H-Bridge Motor Driver

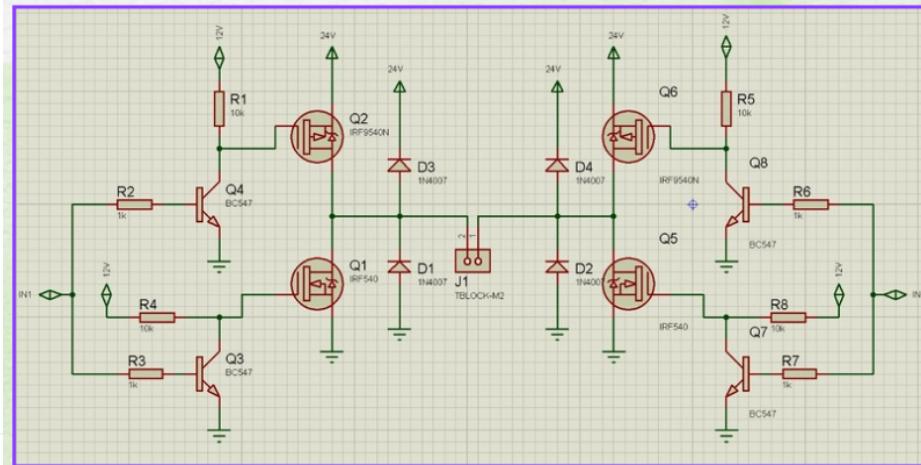


Figure 6: H-bridge circuit after redesigning

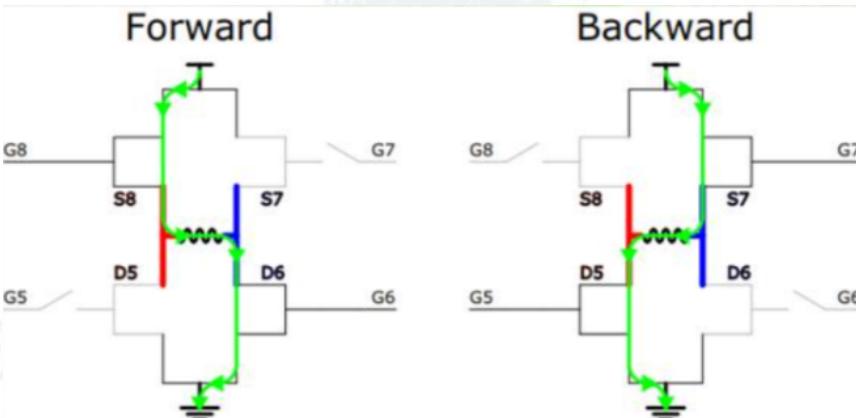


Figure 7: Bi-directional Flow Depicting in the H-bridge Circuit by the Motor

3. Diode Current Handling:

- 1N4007 diodes:
 - Max continuous current = 1 A
 - Peak surge current = 30 A

4. Switching Speed Considerations:

- For BC547:
 - Turn-on/off time \approx 100 ns
 - Switching frequency limit \approx 1 MHz

4.3 Design Rationale

- Mixed Signal/Power Design:
 - BC547 for control/logic functions
 - IRF540/IRF9540N for power switching
- Complementary Topology:
 - NPN/PNP combination enables push-pull operation
- Protection Features:

Table 3: Component Specifications and Functions (Part 1)

Component	Value/Type	Purpose and Characteristics
Resistor R1	10 kΩ	<ul style="list-style-type: none"> Base current limiting resistor Calculation: <ul style="list-style-type: none"> $I_b = \frac{12V - 0.7V}{10k\Omega} = 1.13 \text{ mA}$ For $\beta = 100$: $I_c \approx 113 \text{ mA}$
Transistor Q2,Q6	IRF9540N	<ul style="list-style-type: none"> Power MOSFET (N-channel) V_{DS}: 40 V, I_D: 4 A $R_{DS(on)}$: <0.1 Ω
Resistor R2	1K	Placeholder for future modifications
Transistor Q4,Q4,Q7,Q8	BC547	<ul style="list-style-type: none"> General purpose NPN V_{CEO}: 45 V, I_C: 100 mA

Table 4: Component Specifications and Functions (Part 2)

Component	Value/Type	Purpose and Characteristics
Resistor R3	1K	Same as R2
Resistor R4	10 kΩ	<ul style="list-style-type: none"> Pull-up/pull-down resistor Base current limiting
Transistor Q5,Q1	IRF540	<ul style="list-style-type: none"> Power Mosfet(P-channel) V_{CEO}: -40 V, I_C: -4 A

- 1N4007 diodes provide flyback protection
- 10 kΩ resistors prevent excessive base current

- Scalability:**
 - Multiple parallel transistors suggest high-current capability
 - Unpopulated resistors allow for circuit tuning
- Voltage Requirements:**
 - Component ratings suggest 12 V to 24 V operation
 - 1N4007 diodes allow for high voltage spike handling

Component Analysis

4.4 Resistor R1 (10 kΩ)

- Base Current Calculation for BC547 (Q4):**

$$h_{FE} = 100 \text{ (minimum guaranteed)}$$

$$I_C = 100 \text{ mA (max for BC547)}$$

$$I_B = \frac{I_C}{h_{FE}} = \frac{100 \text{ mA}}{100} = 1 \text{ mA}$$

$$R1 = \frac{V_{CC} - V_{BE}}{I_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{1 \text{ mA}} = 11.3 \text{ kΩ}$$

→ Standard 10 kΩ chosen

- **Purpose:** Limits base current to 1.13 mA (safe for BC547)
- **Trade-off:**
 - Higher values reduce drive capability
 - Lower values risk overdriving transistor

4.5 Transistor Q2 (IRF540N)

- **Parameters:**
 - $V_{DS} = 40\text{ V}$ (matches 12 V system with margin)
 - $I_D = 4\text{ A}$ (sufficient for power switching)
 - $R_{DS(on)} \approx 0.1\Omega$ (low conduction losses)
- **Selection Rationale:**
 - Handles 4× more current than BC547
 - Low gate drive requirements (compatible with BC547)
 - TO-220 package for heat dissipation

4.6 Resistors R2/R3 (1K)

- **Design Flexibility:**
 - Placeholders for current sensing (e.g., 1Ω resistors)
 - Allow for gain adjustment in differential pairs
 - Potential base stopper resistors (100Ω to 1Ω - $1\text{k}\Omega$)

4.7 Transistors Q3/Q4 (BC547)

- **Technical Justification:**
 - $V_{CEO} = 45\text{ V} > 12\text{ V}$ system
 - $I_C = 100\text{ mA}$ sufficient for control
 - $h_{FE} = 110 - 800$ provides good amplification
 - $f_T = 300\text{ MHz}$ for fast switching
- **Cost Optimization:**
 - 0.02/unit vs 0.50 for similar FETs

Power Stage Design

4.8 Resistor R4 (10 kΩ)

- **Pull-up/Pull-down Calculation:**

For 100 μA leakage:

$$V_{drop} = I \times R = 100 \mu\text{A} \times 10 \text{k}\Omega = 1 \text{ V}$$

$$P = I^2 R = (100 \mu\text{A})^2 \times 10 \text{k}\Omega = 0.1 \text{ mW}$$

- **Noise Consideration:**
 - Low enough to prevent floating inputs
 - High enough to not overload drivers

4.9 Power Transistors Q5/Q7/Q9/Q10

- Current Sharing Calculation (4 parallel):

$$I_{total} = 4 \times 4 \text{ A} = 16 \text{ A}$$
$$\Delta I = \pm 10\% \rightarrow 0.4 \text{ A}$$
$$R_e = \frac{\Delta V_{BE}}{\Delta I} = \frac{0.05 \text{ V}}{0.4 \text{ A}} \approx 0.125 \Omega$$

→ Standard 0.1 Ω used

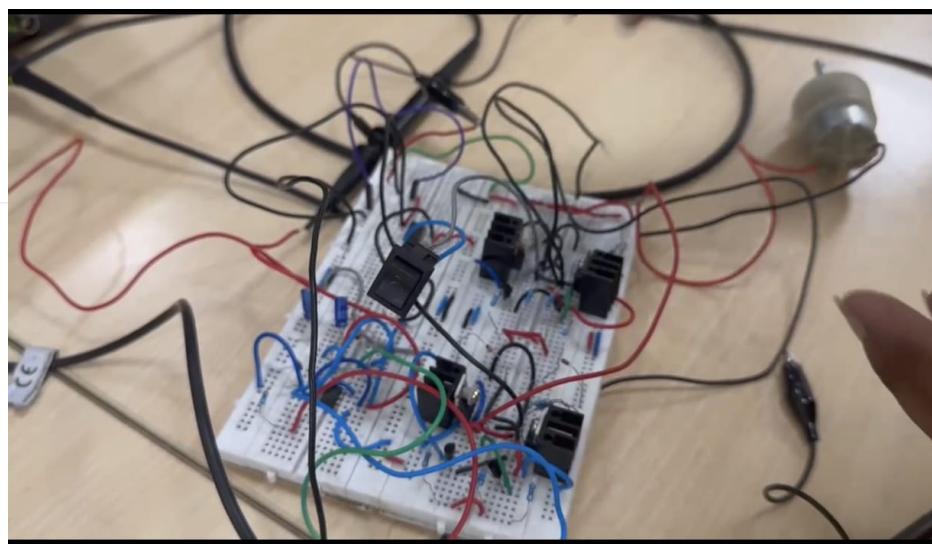


Figure 8: Final Hardware Implementation of the circuit

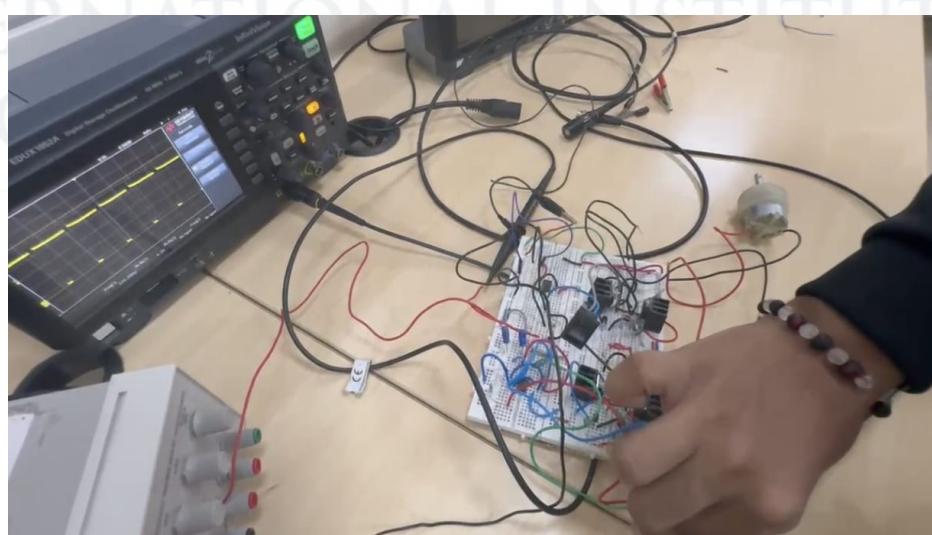


Figure 9: Duty Cycle changing with the Potentiometer

* How exactly is a potentiometer working?

$$\frac{V_o}{V_p} = \frac{R_{out}}{R_{in} + R_{out}}$$

$$V_o = V_p \cdot \frac{10k}{0.001k} \times 12$$

$$V_o = 10k \cdot \frac{10}{0.001} \cdot 12$$

$$= 10^3 \cdot 10^3 \cdot 12$$

$$= 10^6 \cdot 12$$

$$= 12 \cdot 10^6$$

$$= 12 \text{ M}$$

$$V_{out} = V_{in} \cdot \frac{R_{out}}{R_{in} + R_{out}}$$

$$= V_{in} \cdot \frac{10.000001k - R_{in}}{R_{in} + 10.000001k}$$

$$= V_{in} \cdot \frac{10.000001k}{10.000001k}$$

$$V_{out} = V_{in}$$

when $R_{in} \ll R_{out}$

$$V_{out} = 0$$

when $R_{in} \gg R_{out}$

$$V_{out} = 12, 9, 6, 3, 0$$

$$0, 8, 4, 6, 8, 10, 12$$

Figure 10: Some theoretical calculations while doing the project

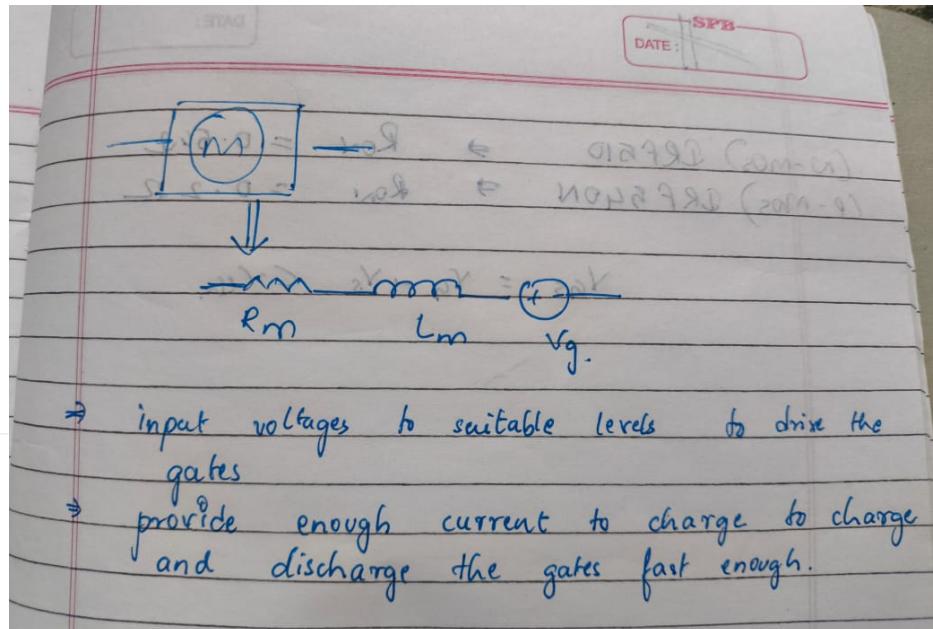


Figure 11: Some theoretical calculations while doing the project

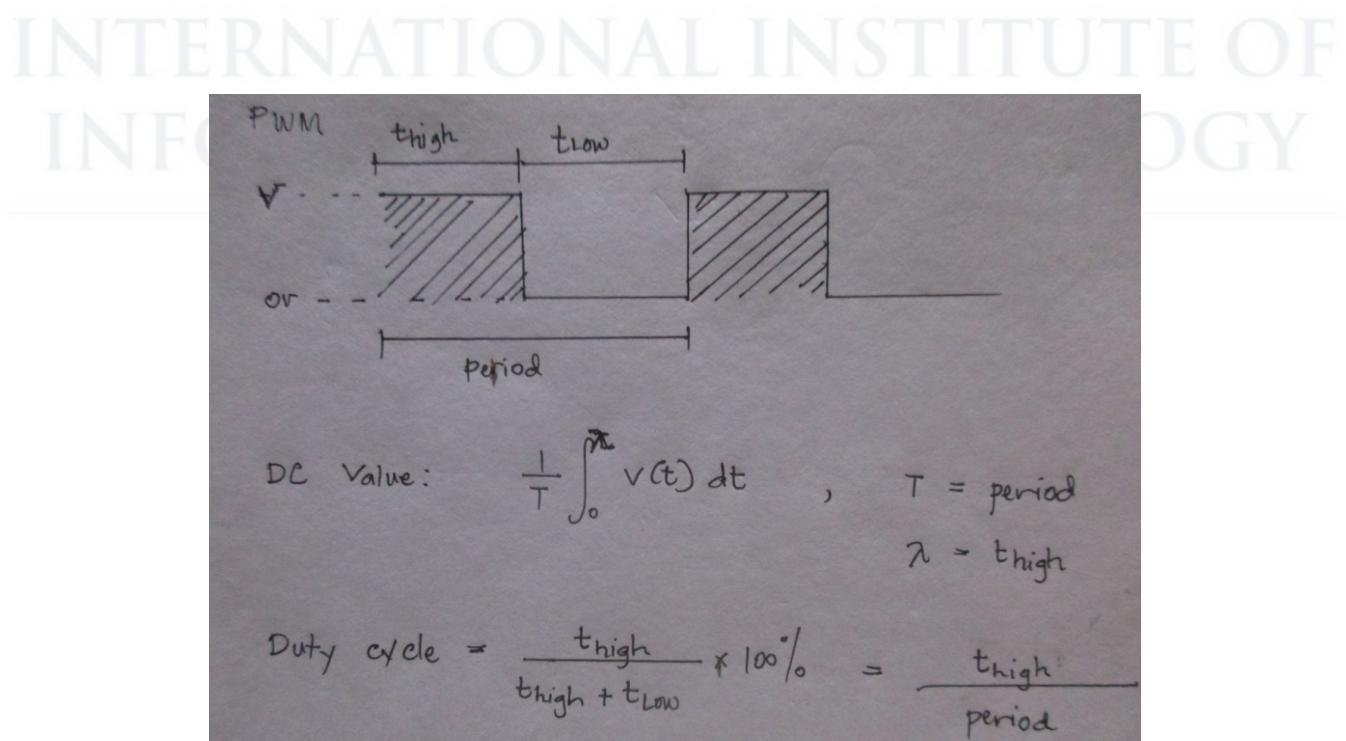


Figure 12: Duty cycle calculations

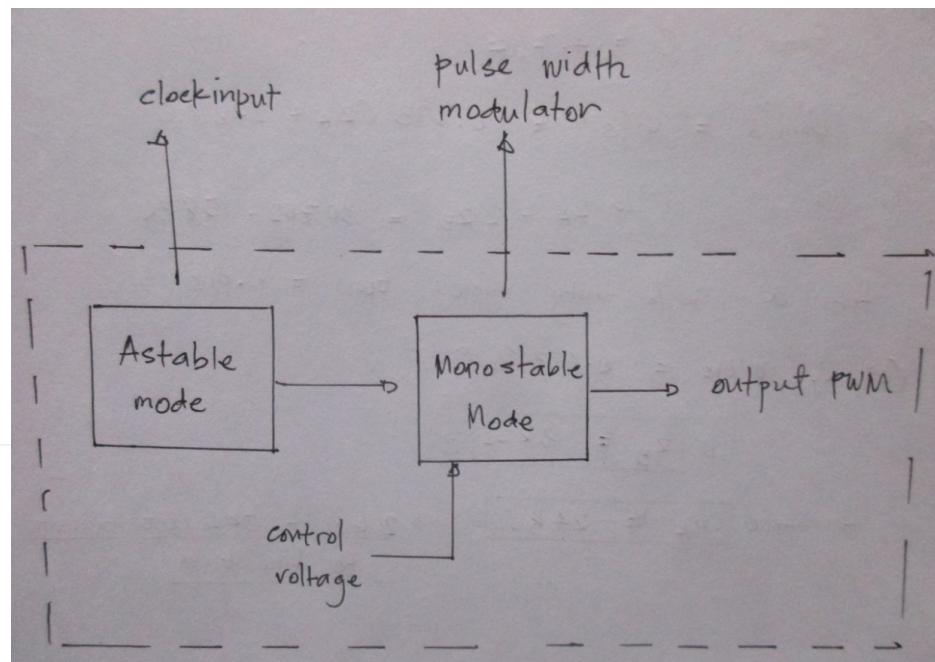


Figure 13: different 555 timer design motivation

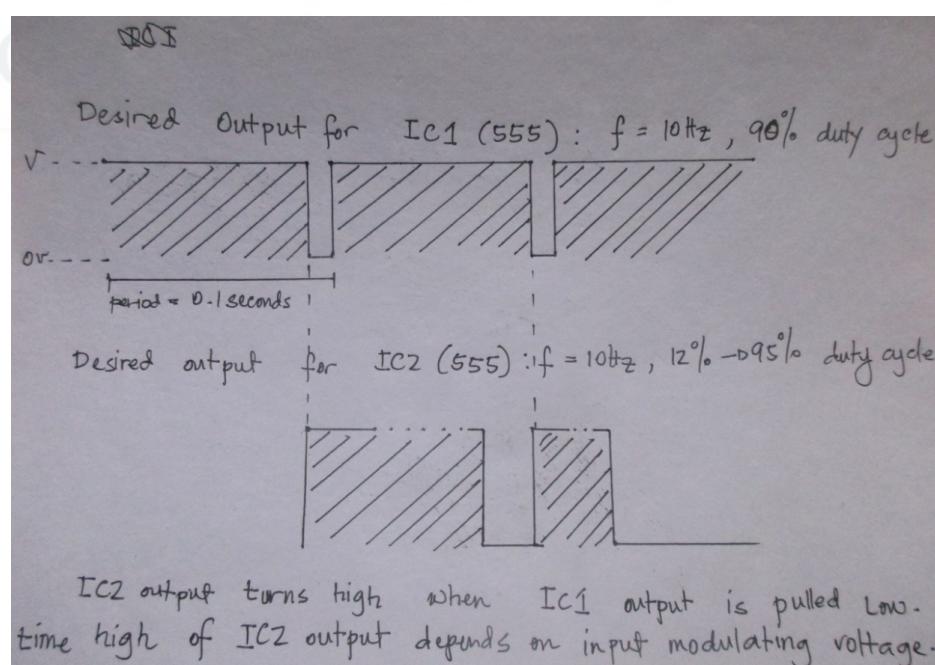


Figure 14: Some theoretical calculations